


淡江大學八十七學年度日間部轉學生入學考試試題

系別：電機工程學系三年級


科目：電子學

本試題共 1 頁

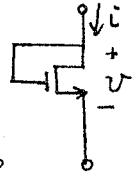1. For the diode-connected enhancement MOSFET of Fig. 1, find an expression for its incremental resistance r at $V = 2V_t$. Neglect the small effect of r_o . Evaluate r for the case $V_t = 1V$, $\mu_n C_{ox} = 20 \mu A/V^2$, $W = 6 \mu m$ and $L = 30 \mu m$.




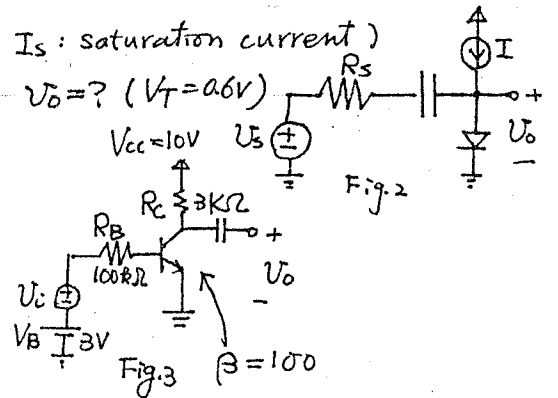2. In the circuit shown in Fig. 2, I is a dc current and V_s is a sinusoidal signal. Use the diode small signal model to show that the signal component of the output signal voltage $V_o = ?$ (in terms of V_T , R_s , I , V_s assuming $i-v$ of diode is $i \approx I_s e^{v/V_T}$, I_s : saturation current)
 ② If $V_s = 10mV$, $I = 1mA$, $R_s = 1K\Omega$, Find $V_o = ?$ ($V_T = 60mV$)



3. Determine the voltage gain of Fig. 3, $\frac{V_o}{V_i} = ?$
 (20%) (V_o, V_i are small signal)

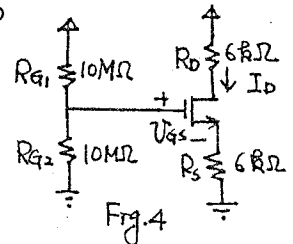4. Determine the circuit shown in Fig. 4, $V_{GS} = ?$ $I_D = ?$
 (20%)



5. Consider the current mirror circuit of Fig. 5, with $V_{SS} = -5V$, $I_{REF} = 10 \mu A$, $V_T = 1V$, $\mu_n C_{ox} = 20 \mu A/V^2$, $V_A = 20V$, $L = 10 \mu m$, $W = 40 \mu m$ for Q_1, Q_2, Q_3, Q_4 . Find ① the output resistance ② the lowest allowable output voltage.

