

淡江大學八十七學年度日間部轉學生入學考試試題


系別：電機工程學系三年級

科目：電路學


本試題共 / 頁

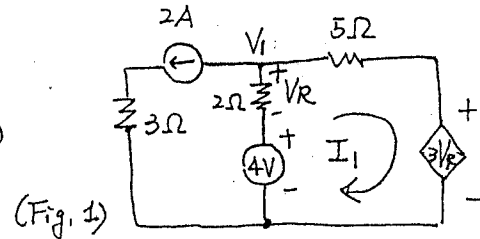1. The circuit shown in Fig 1.


- 20% (a) Find the current I_1
 (b) Determine the power supplied (or absorbed) by the controlled-voltage source



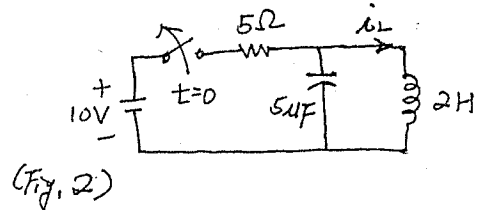
2. The circuit shown in Fig. 2 is under steady state and the switch is opened at $t=0$. Find the frequency and magnitude of the current i_L



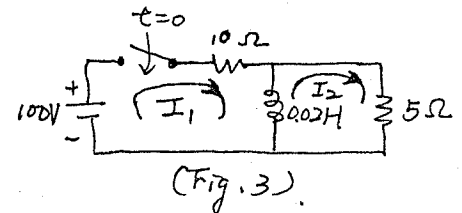3. The switch shown in Fig. 3 is closed at $t=0$. using Laplace transform method to find the currents I_1 and I_2 for $t > 0$



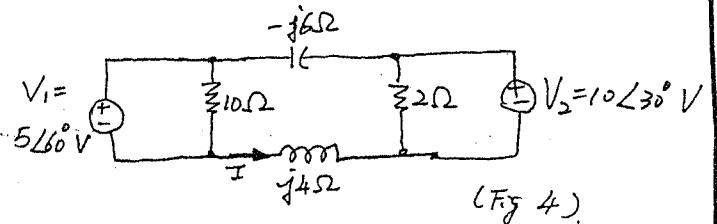4. Determine the current in the $j4\Omega$ inductor of the circuit of Fig 4.



5. Design an RL high-pass filter having a cutoff frequency of 2kHz.

- 20% (a) Let $R = 4k\Omega$, find $L = ? H$.
 (b) determine V_{out} at 100 Hz, 500 Hz and 100kHz for a 100V input.