

53-1

淡江大學九十三學年度轉學生招生考試試題

系別：電機工程學系三年級


科目：電子學

准帶項目請打「○」否則打「×」
簡單型計算機


節次：7月14日第1節
本試題共2頁

本試題雙面印製

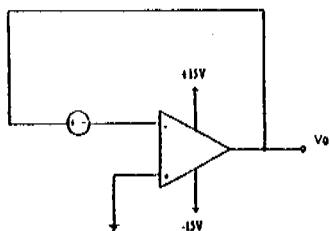
1. 20% The input voltage of the following op amp is 0.01mV. The input bias current is 0A, and the open loop gain is -200. What is V_o ?



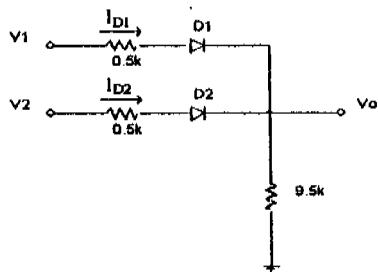
2. 20% The diodes in the following circuit have piecewise linear parameters of $V_r = 0.6V$ and $I_f = 0$. Determine the output voltage V_o , the diode currents I_{D1} , and I_{D2} for the following input conditions: $V_1=10V$ and $V_2=0V$.



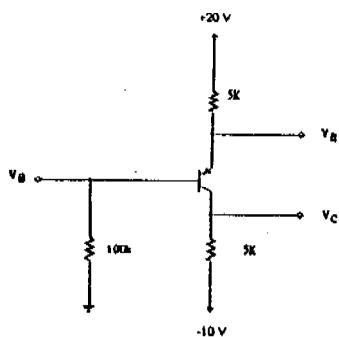3. 20% In the following circuit, assume $V_B=1V$ and $V_E=1.7V$. Solve α , β , and V_C ?



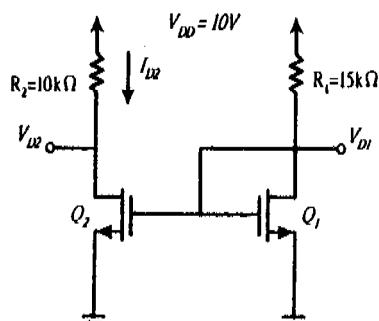4. 20% Q_1 and Q_2 have the same parameters as follows: $V_t=2V$, $\mu_n C_{ox}=20\mu\text{A}/\text{V}^2$, $L=10\mu\text{m}$, $W=100\mu\text{m}$, and $\lambda=0$. Find V_{D1} , V_{D2} , and I_{D2} .



淡江大學九十三學年度轉學生招生考試試題 53-2

系別：電機工程學系三年級

科目：電子學

准備項目請打「○」否則打「x」	
	簡單型計算機

節次：7月14日第1節
本試題共2頁

5. 20% A cascade amplifier is shown in the following figure, in which both MOSFETs are identical. The relevant parameters include the threshold voltage $V_{TH} = 1.2V$ and the conduction parameter $K=0.8mA/V^2$. The resistances of all capacitors are neglected. Find V_{GSI} , I_{DQ1} , g_m , and V_O/V_S .

