

淡江大學九十四學年度轉學生招生考試試題

系別：電機工程學系三年級 科目：電子學

准帶項目請打「V」	
<input checked="" type="checkbox"/>	簡單型計算機


節次：7 月 13 日第 1 節
本試題共 3 頁 - 1 /

本試題雙面印製

※ 請務必依序作答 ※


10%

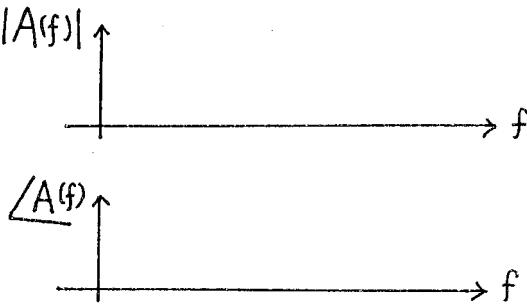1. Draw the ideal amplitude and phase responses of an ideal voltage amplifier.



15%

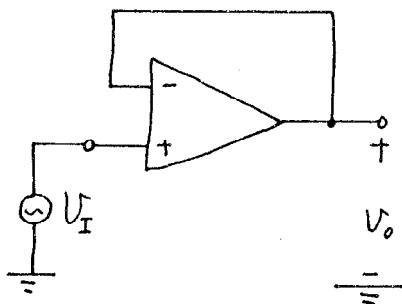2. Please derive the gain expression of the voltage follower below. (Assume the OP AMP is ideal except that it has a finite gain A)



15%

3. When a load resistor of $2\text{k}\Omega$ is connected to a voltage amplifier, the output voltage V_O would decrease 20%. What is the value of the amplifier output resistance R_o ?

淡江大學九十四學年度轉學生招生考試試題

系別：電機工程學系三年級 科目：電子學


准帶項目請打「V」	
	簡單型計算機

節次：月日第節

本試題共 3 頁 - 2

10%

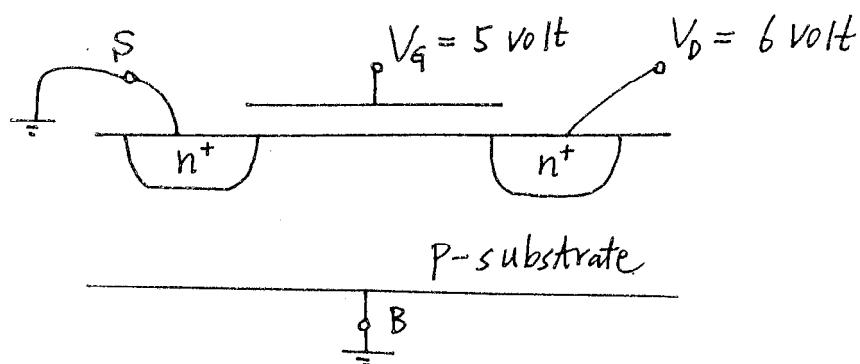4. Draw the channel shape in the MOS figure below. (Assume the threshold voltage $V_t = 2 \text{ volt}$)



10%


5. A transistor with $\beta = 150$ is biased to operate at a dc collector current $I_c = 1.5 \text{ mA}$. Find the values of g_m , r_e and V_e . (Assume room temperature).

10%

6. (a) What is the body effect in a MOS amplifier?
 (b) How to avoid it?

10%

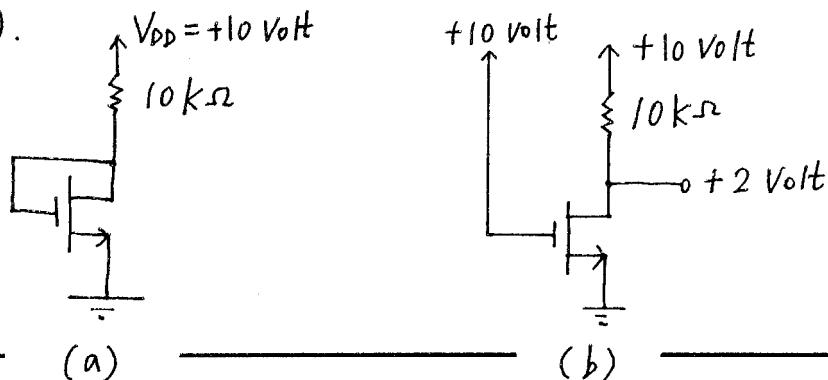7. In what region is the MOSFET operated in the following figures (a) and (b).



淡江大學九十四學年度轉學生招生考試試題

系別：電機工程學系三年級 科目：電子學


准帶項目請打「V」	
	簡單型計算機

節次：月日第節

本試題共 3 頁 - 1

10%

8. In the circuit below, if the base width W_B of the transistor is enlarged conceptually, how would the base current $|I_B|$ change?

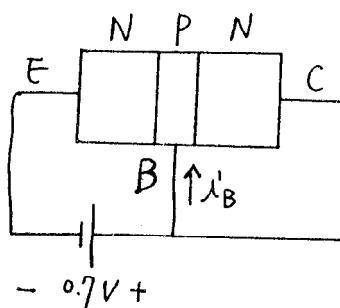

10%

9. For the op-AMP circuit below, when a dc voltage $V_I = 0.01$ Volt is applied, what is the steady output voltage V_o ?

