

淡江大學九十四學年度轉學生招生考試試題

系別：電機工程學系三年級 科目：電路學

准帶項目請打「V」	
V	簡單型計算機

節次：7月13日第3節
本試題共1頁

1. The switch in the circuit of Fig. 1 has been closed for a long time. It is opened at $t = 0$. Find $v_o(t)$ for $t > 0$. (25%)

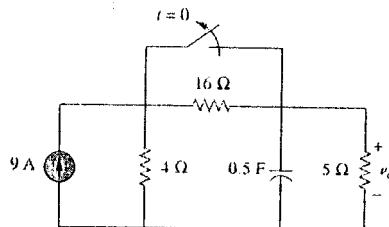


Fig. 1

2. Find the complete response $i(t)$ for $t > 0$ in the circuit of Fig. 2. (25%)

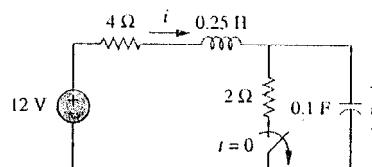


Fig. 2

3. In the circuit of Fig. 3, let $R_1 = R_2 = 1\Omega$, $C_1 = 0.2\text{ F}$, and $C_2 = 0.1\text{ F}$. (25%)

- (a) Find $H(j\omega) = V_o(j\omega)/V_i(j\omega)$
 (b) Find the frequency response. (i.e., plot the magnitude and phase of $H(j\omega)$ versus ω , respectively.)

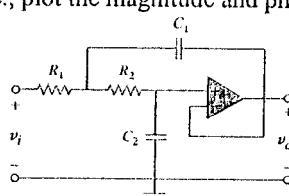


Fig. 3

4. Find the complete response $v_o(t)$ for $t > 0$, in the circuit of Fig. 4 if $v_s(t) = 10u(t)\text{ V}$ and $v_o(0) = -5\text{ V}$. (25%)

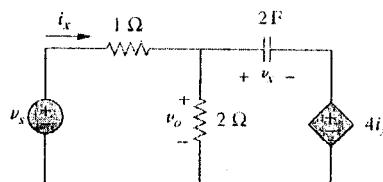


Fig. 4