

淡江大學 104 學年度日間部轉學生招生考試試題

系別：電機工程學系三年級

科目：電子學

考試日期：7月26日(星期日) 第1節

本試題共 5 大題， 2 頁

本試題雙面印刷

1. 20% Assuming $V_{in} = V_P \sin \omega t$, plot the output waveform of the circuit depicted in Fig. 1 for an initial condition of +0.5V across C_1 . Assume $V_P = 5V$.

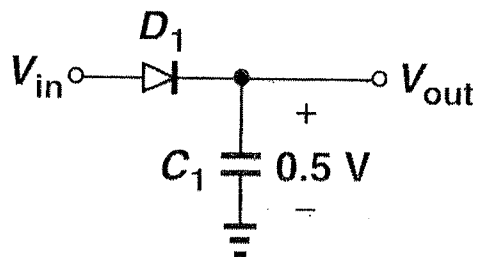


Fig. 1

2. 20% Find the emitter, base, and collector voltages and currents of the following circuit. Use $\beta = 30$, but assume $|V_{BE}| = 0.7V$ independent of the current level.

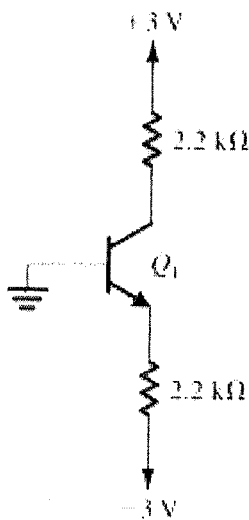


Fig. 2

3. 20% In the BJT, please present the parameters of g_m , r_{π} and r_o in terms of I_C , β , V_T , and V_A .
4. 20% A Common-Emitter (CE) amplifier utilizes a BJT with $\beta = 100$ biased at $I_C = 0.5mA$ and has a collector resistance $R_C = 10 k\Omega$ and a resistance $R_e = 150\Omega$ connected in the emitter. Find R_{in} , $A_{vo} = v_o/v_i$, and R_o . Assume $V_A = \infty$.

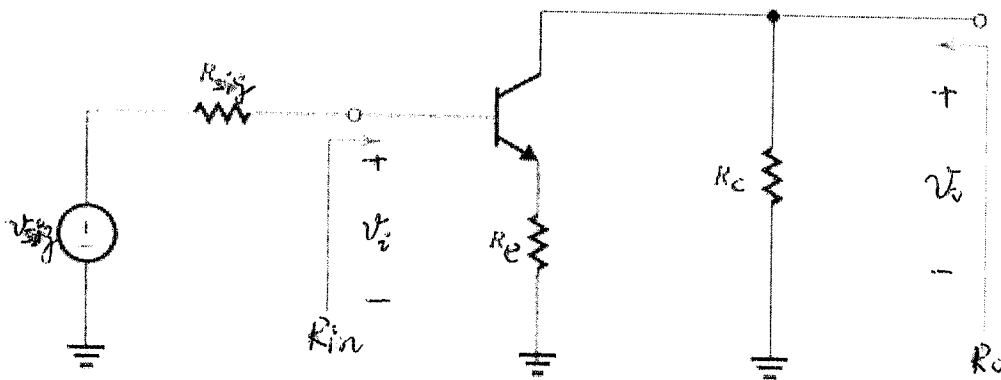


Fig. 4

背面尚有試題

淡江大學 104 學年度日間部轉學生招生考試試題

4-2

系別：電機工程學系三年級

科目：電子學

考試日期：7月26日(星期日) 第1節

本試題共 5 大題， 2 頁

5. 20% An emitter follower with a BJT biased at $I_C = 1$ mA and having $\beta = 100$ is connected between a source with $R_{sig} = 20$ k Ω and a load $R_L = 1$ k Ω . Find R_{in} , v_b/v_{sig} , and v_o/v_{sig} .

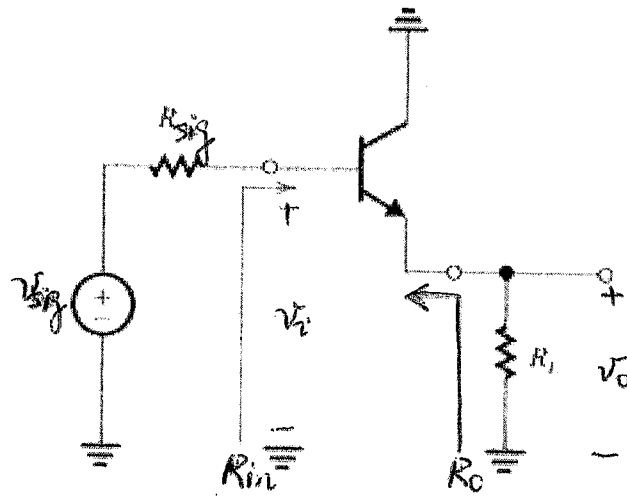


Fig. 5