

淡江大學 95 學年度進修學士班轉學生招生考試試題

系別：電機工程學系三年級

科目：電子學

13-1

准帶項目請打「V」	
✓	簡單型計算機

本試題共 2 頁一

1. Assume that the operational amplifier in the circuit of Fig. 1 is ideal. Derive the voltage gain V_o/V_i of this noninverting amplifier. (20%)

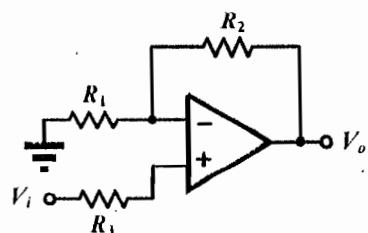


Fig. 1

2. Assume that the diodes D_1 and D_2 in the circuit of Fig. 2 are ideal, find the values of the labeled voltage V and current I . (20%)

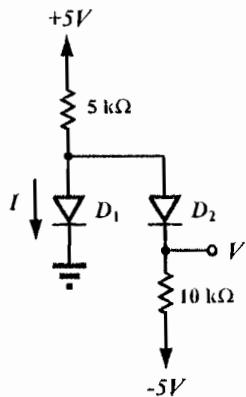


Fig. 2

3. For the circuit in Fig. 3, $V_m = 1V$, $\mu_n C_{ox} = 20 \mu\text{A}/\text{V}^2$, $L = 10 \mu\text{m}$, and $W = 30 \mu\text{m}$. Neglect the channel length modulation and body effect, find the labeled voltage V_2 and current I_L . (20%)

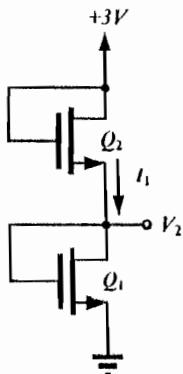


Fig. 3

淡江大學 95 學年度進修學士班轉學生招生考試試題

系別：電機工程學系三年級

科目：電子學

13-2

准備項目請打「V」	
✓	簡單型計算機

本試題共 2 頁

4. For the circuit in Fig. 4, the BJT has a common-emitter current gain $\beta = 100$, $V_{BE}=0.7V$, and $R_B=100k\Omega$. Find the dc currents I_B , I_C , and I_E , and dc voltage V_B , V_C , and V_E . (20%)

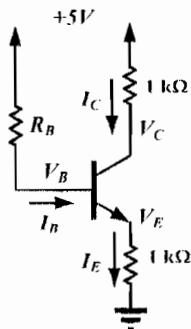


Fig. 4

5. For the NMOS amplifier in Fig. 4, replace the transistor with its equivalent small-signal model, ignore the channel length modulation and body effect. Derive expressions for the voltage gains v_s/v_i and v_d/v_i . [utilize g_m to represent the transconductance of transistor] (20%)

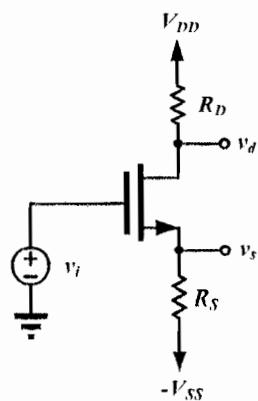


Fig. 5