

淡江大學 98 學年度進修學士班轉學生招生考試試題

系別：電機工程學系三年級

科目：電子學

准帶項目請打「V」	
✓	計算機

本試題共 5 大題， 2 頁

1. 20% Consider the difference-amplifier circuit of Fig. 1 (the op amp is ideal) for the case $R_1 = R_3 = 2\text{k}\Omega$ and $R_2 = R_4 = 200\text{k}\Omega$.

- (a) Find the value of the differential gain $A_d = (v_1 - v_2)/v_o$.
- (b) Find the value of the differential input resistance R_{id} and the output resistance R_o .

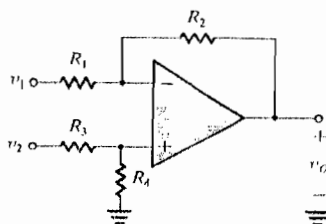


Fig. 1

2. 20% Find the values of the V and I as shown in Fig. 2. Assume the diodes are ideal.

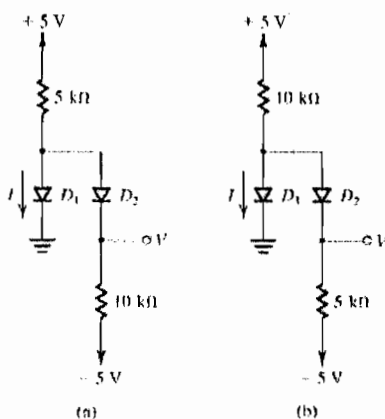


Fig. 2

3. 20% Assume $\lambda = 0$. In Fig. 3, what are the drain currents, I_D , in saturation and triode regions respectively of an NMOS transistor?

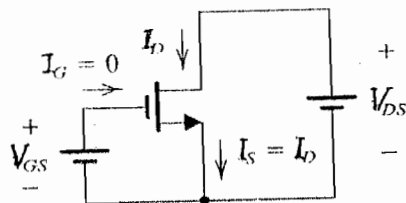


Fig. 3

本試題雙面印刷

淡江大學 98 學年度進修學士班轉學生招生考試試題

系別：電機工程學系三年級

科目：電 子 學

准帶項目請打「V」	
V	計算機

本試題共 5 大題， 2 頁

4. 20% In Fig. 4, the transistor has $V_t = 1.5\text{V}$, $K_n'(W/L) = 0.25\text{mA/V}^2$, and $V_A = 50\text{V}$. Assume the coupling capacitor to be sufficiently large so as to act as short circuits as the signal frequencies of interest. Find the small-signal voltage gain (A_v) and input resistance (R_{in}).

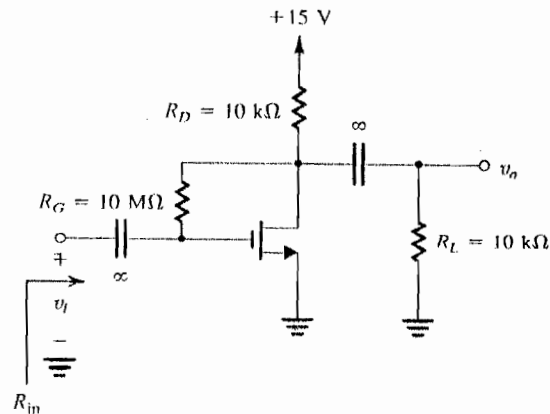


Fig. 4

5. 20% Analyze Fig. 5 to find I_C , I_B , V_C , and V_B . Assume $\beta = 100$.

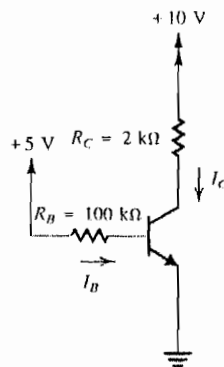


Fig. 5