

淡江大學 99 學年度進修學士班轉學生招生考試試題

系別：電機工程學系三年級

科目：電 子 學

本試題共 7 大題， 2 頁

1. 15% Fig. 1 shows a parallel resistor-diode combination. IF $I_S = 3 \times 10^{-16} \text{ A}$, calculate V_{D1} for $I_X = 1 \text{ mA}$, 2 mA , and 4 mA .

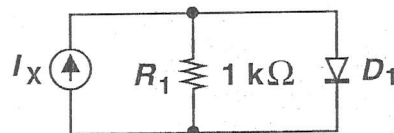


Fig. 1

2. 20% Plot the input/output characteristics of the circuits shown in Fig. 2 using an ideal model for the diodes.

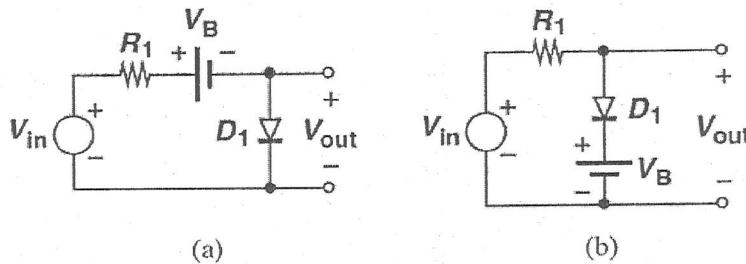


Fig. 2

3. 15% Consider the circuit shown in Fig. 3, where $I_S = 5 \times 10^{-16} \text{ A}$ and $V_A = \infty$. If V_B is chosen to forward-bias the base-collector junction by 200 mV , what is the collector current?

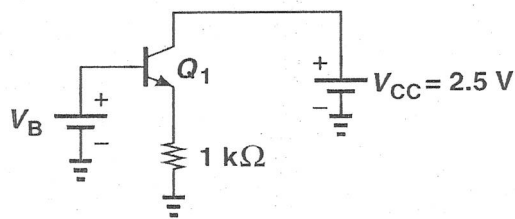


Fig. 3

4. 15% What are
- Common collector amplifier?
 - Common base amplifier?
 - Emitter follower?

本試題雙面印刷

背面尚有試題

5. 10% Determine the voltage gain of Fig. 5. Assume $I_S = 7 \times 10^{-16} \text{ A}$, $\beta = 100$, and $V_A = 5 \text{ V}$. (But for bias calculation, assume $V_A = \infty$). Also, assume the capacitors are very large.

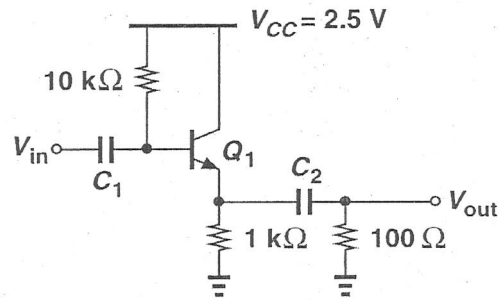


Fig. 5

6. 10% Compute the value of W/L for M_1 in Fig. 6 for a bias current of I_1 . Assume $\lambda = 0$. For NMOS, $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, $V_{TH} = 0.4 \text{ V}$.

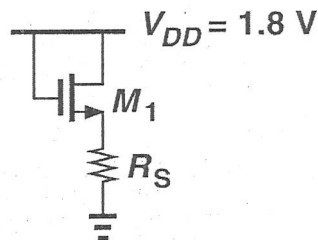


Fig. 6

7. 15% What are
- Common source amplifier?
 - Common gate amplifier?
 - Source follower?