

淡江大學九十四學年度碩士班招生考試試題

95-

系別：機械與機電工程學系 科目：動態系統

准帶項目請打「○」否則打「×」
簡單型計算機
○

本試題共 2 頁 第 1 頁

1. (25%) A mass-pulley system shown in Figure 1 has a rotating wheel of inertia J . Two springs and a damper are connected to the wheel using a cable without slip on the wheel. Where k_1 and k_2 are spring constants, b is the coefficient of viscous friction, d is the diameter of the wheel, x is the displacement of mass m , θ is the rotation angle of the wheel, and $u(t)$ is an input motion.
 - a. Derive the force balance equation for the mass m , the moment balance equation for the wheel, and the displacement equation for x and θ .
 - b. Derive the equation of motion for the system in terms of variable x and the input motion $u(t)$.
 - c. Determine the natural frequency and damping ratio of this second-order system.

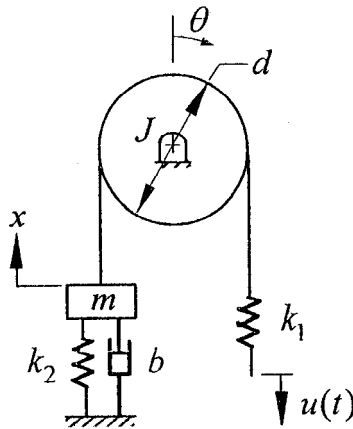


Figure 1 Mass-pulley system

2. (25%) Consider the RLC circuit of Figure 2, which consists of the series connection of a voltage source, $v_s(t)$, a resistor R , an inductor L and a capacitor C .
 - a. Find the transfer function between the capacitor voltage $v_c(t)$ and the input voltage source $v_s(t)$.
 - b. Determine the frequency response, $\frac{v_R(j\omega)}{v_s(j\omega)}$. Also calculate the resonant frequency, if $R=10\Omega$, an inductor $L=5mH$, and a capacitor $C=10\mu F$.

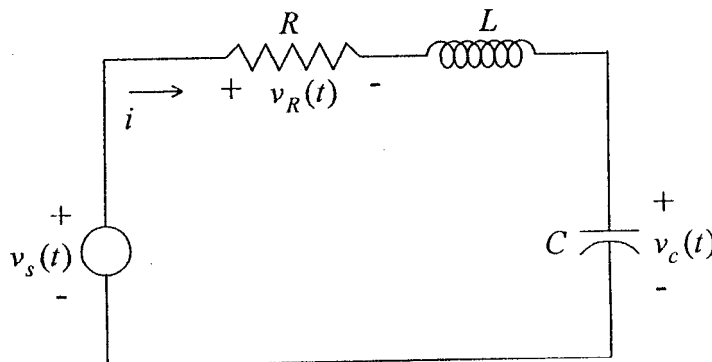


Figure 2 RLC circuit

【注意背面尚有試題】

本試題係由淡江大學機電系提供

淡江大學九十四學年度碩士班招生考試試題

系別：機械與機電工程學系 科目：動態系統

准帶項目請打「○」否則打「×」

簡單型計算機

○

本試題共 2 頁 第 2 頁

3. (25%) A 1000kg boxcar with a velocity 1 m/s approaches an arresting system composed of a linear spring and a viscous damper as shown in Figure 3.
- Derive the equation of motion describing what happens after the car contacts the arresting system.
 - Find the time and distance when the car first time comes to rest. Assume that $k=25\text{N/m}$ and $b=350\text{N sec/m}$.

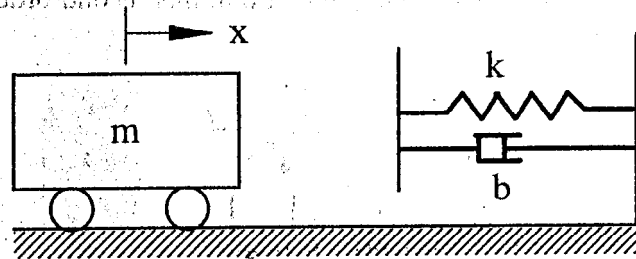


Figure 3 Boxcar

4. (25%) For the circuit shown in Figure 4, assume that the switch S_1 is opened for a long time and closed at $t=0\text{sec}$, then, the circuit can be viewed as a first-order system.
- Determine the capacitor voltage, $v_c(t)$ at $t=0^+\text{sec}$.
 - Derive an expression for the capacitor voltage $v_c(t)$ when $t>0\text{sec}$.
 - What is the time constant, τ , of the circuit for $t>0\text{sec}$?

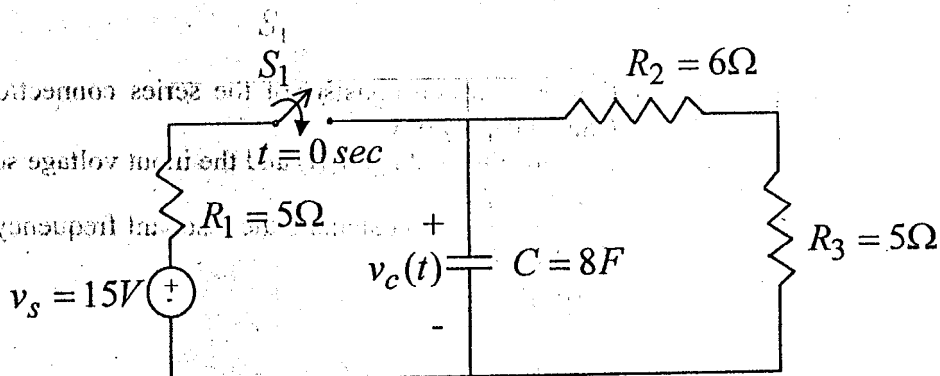


Figure 4 First-order circuit