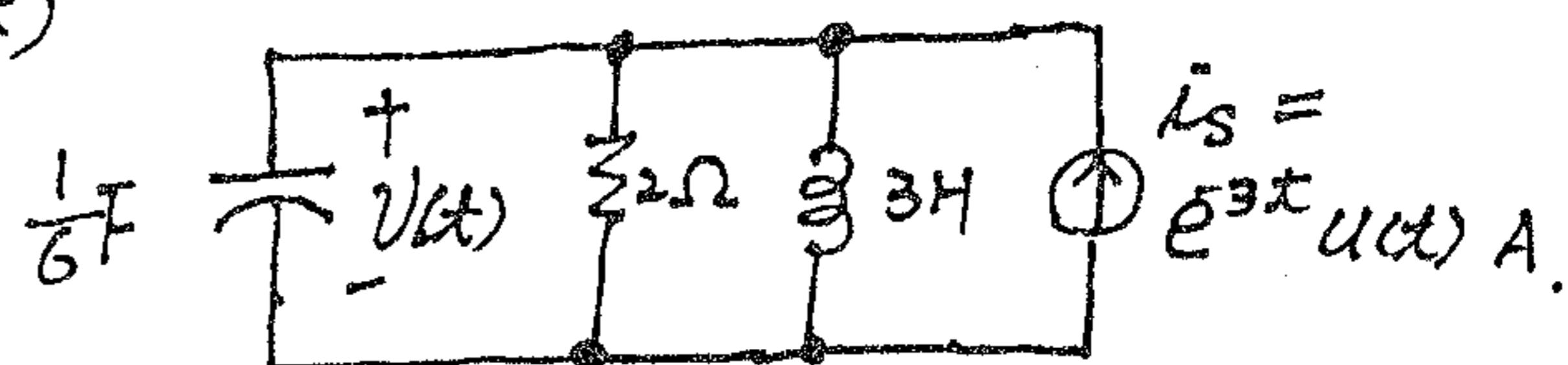


系別：電機工程學系


科目：電路學

本試題共 2 頁 1/2

1. 15% Determine the particular response  $v(t)$  for  $t > 0$  in the second-order circuit.



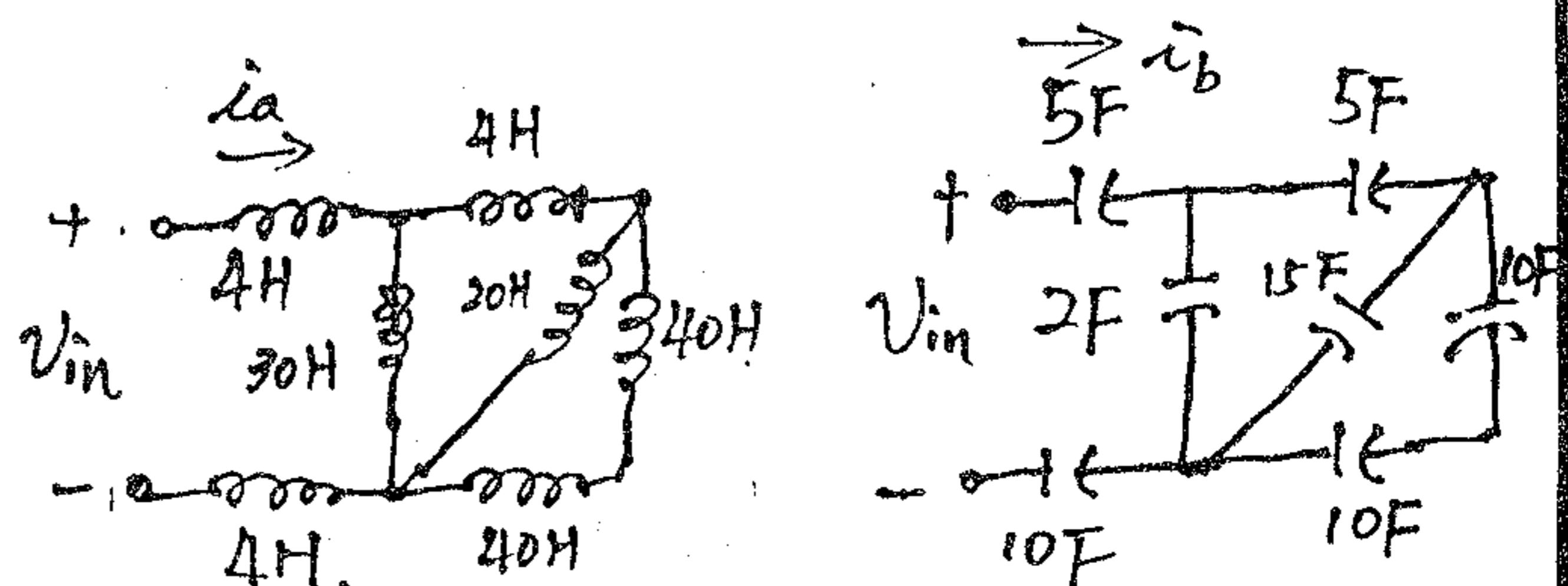2. 10% Calculate the current  $i_a$  and  $i_b$  if  $v_{in} = 40 e^{5t}$



3. 15% The differential equation relating the input  $i(t)$  to the output  $v(t)$  of a circuit is

$$\frac{d^2}{dt^2}v + 4 \frac{d}{dt}v + 3v = \frac{d}{dt}\bar{i} + 2\bar{i}$$

find the impulse response  $h(t)$  of this circuit

4. 20% The current  $i(t)$  in figure (4) is

$$i(t) = A \sin(Bt + C^\circ) - D \text{ (amp)}$$

find  $A$ ,  $B$ ,  $C$ , and  $D$

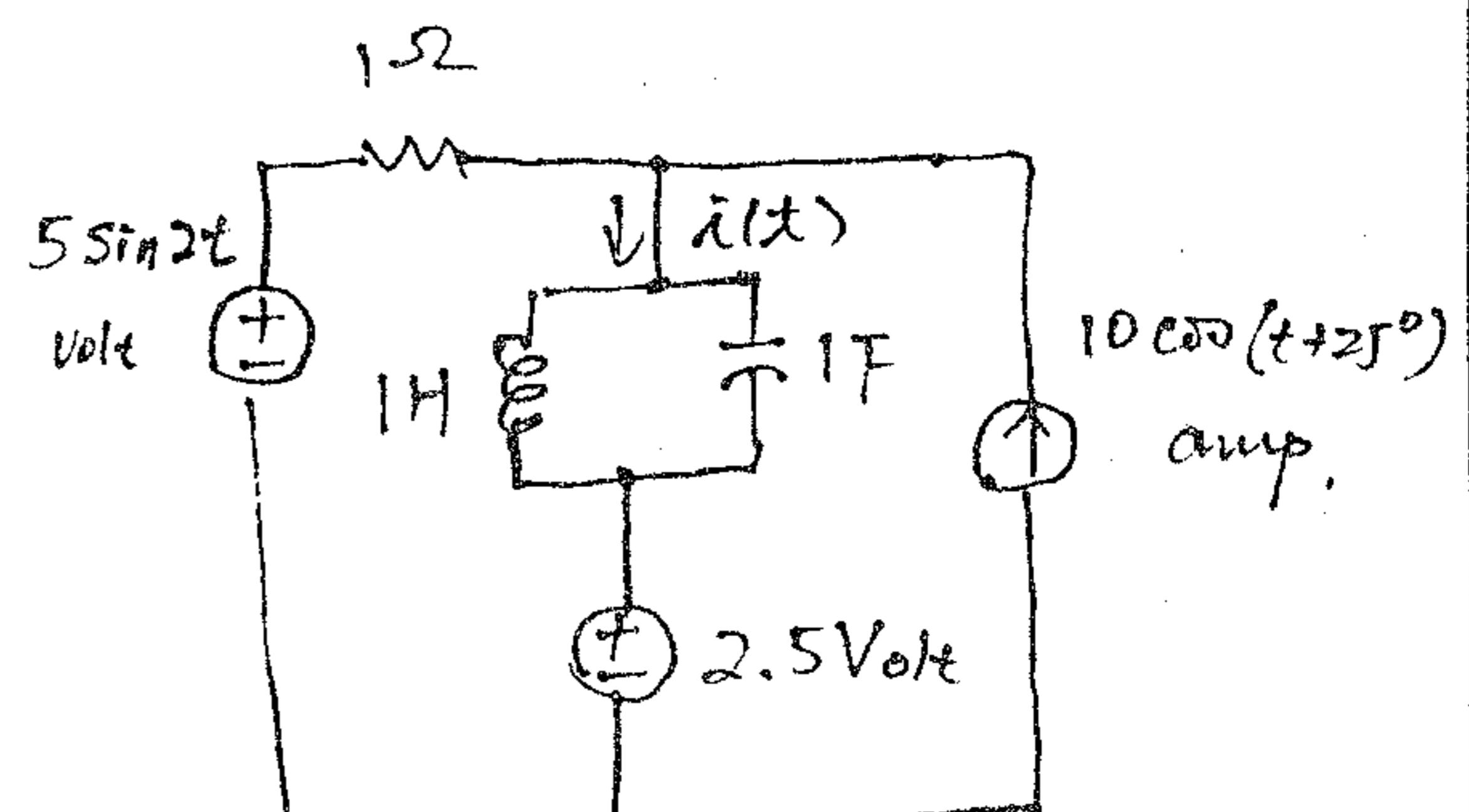


figure (4)

# 淡江大學八十九學年度碩士班招生考試試題

系別：電機工程學系

科目：電路學

本試題共 2 頁 / 2

本試題雙面印製

5. The circuit shown in figure (5)  
 10%  $v(t) = 10 \cos 10t$ , find the  
 (a) power delivered to the resistor  
 (b) average power delivered by the source

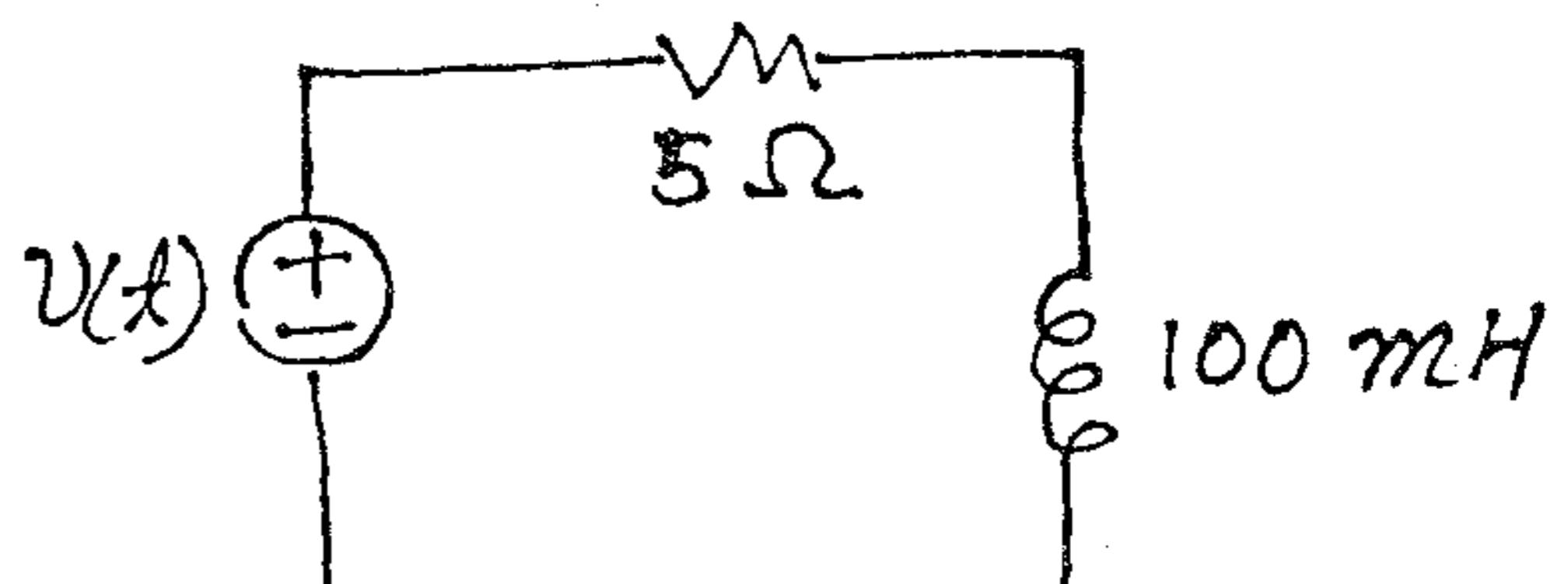


figure (5)

6. For the circuit shown in figure (6,a)  
 20% find the voltage transfer function  
 $H(j\omega) = ?$

and shows the frequency response characteristics as in figures (6.b) & (6.c)

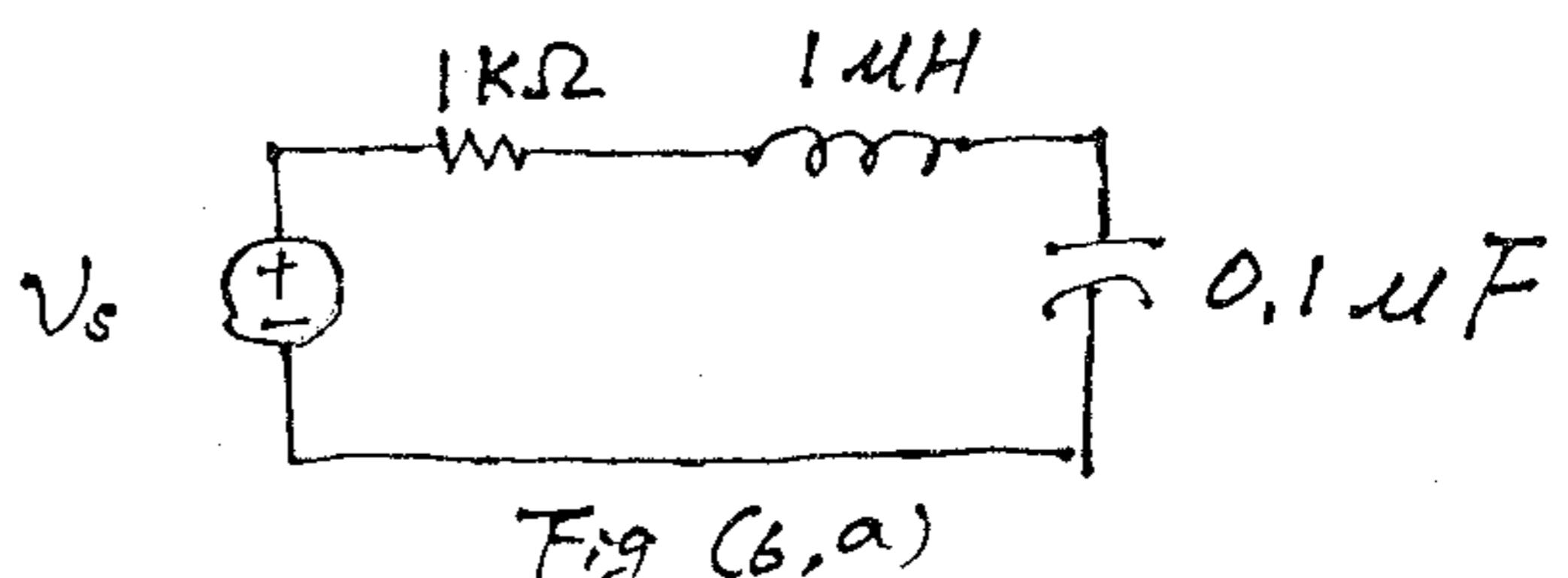


Fig (6.a)

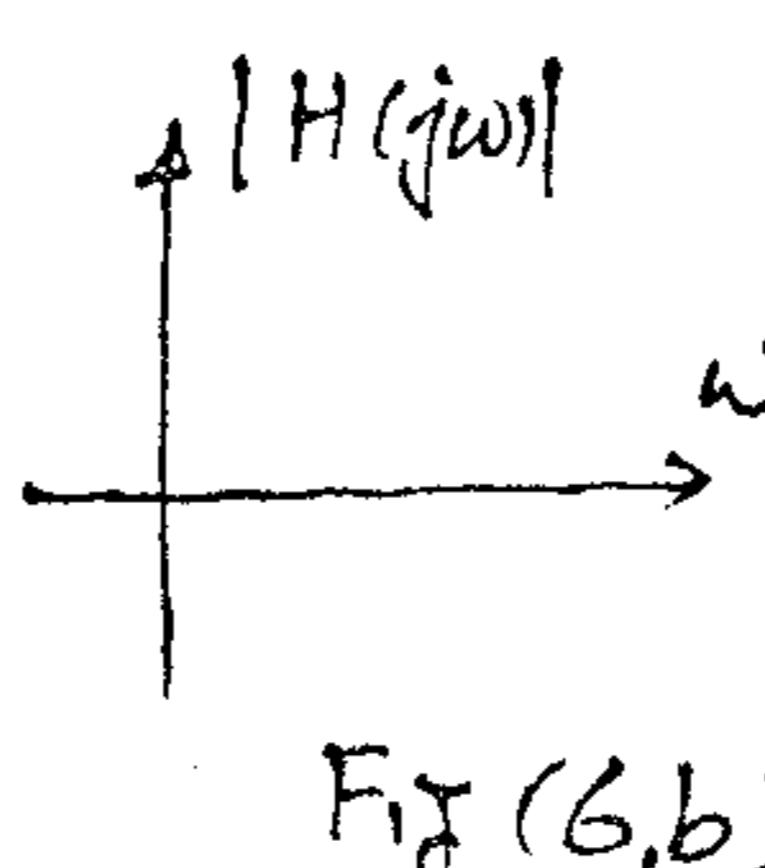


Fig (6.b)

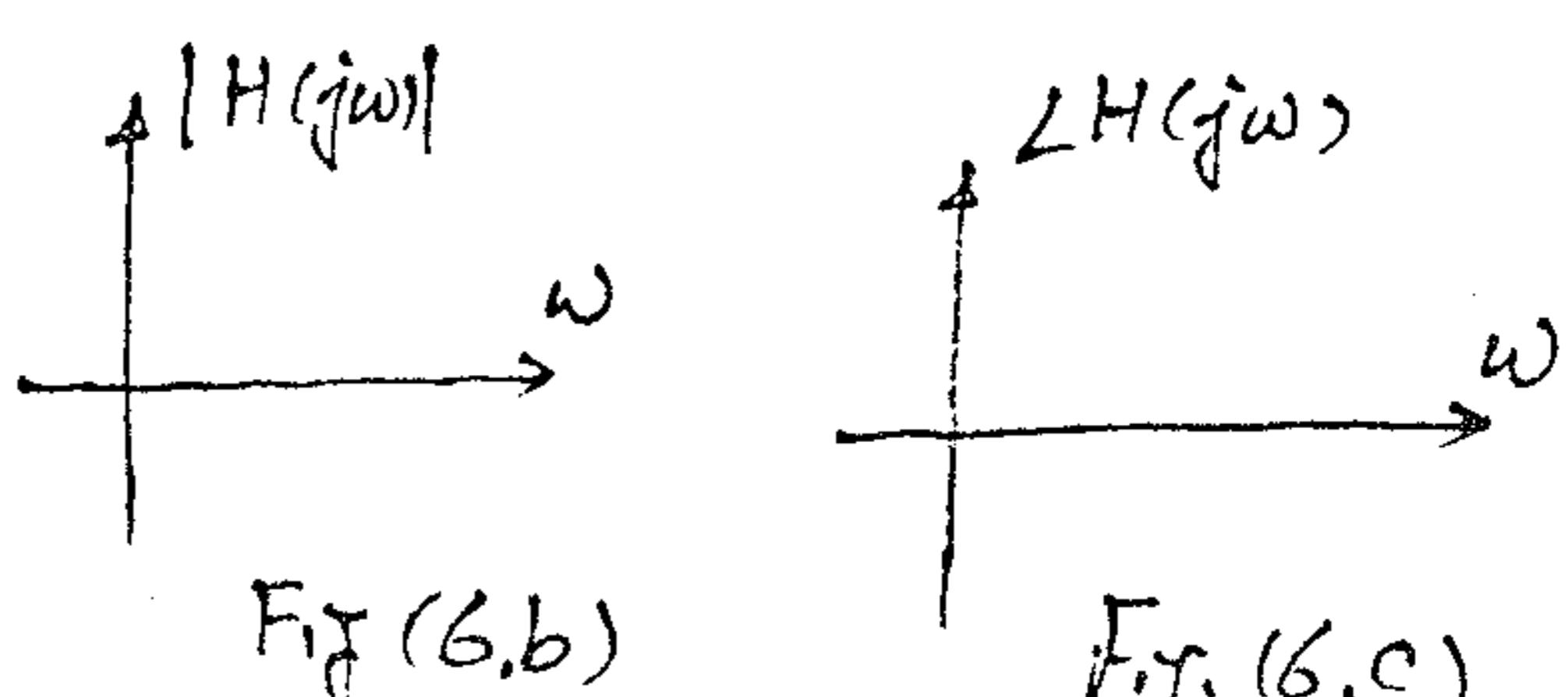


Fig (6.c)

7. For the circuit shown in figure (7,a)  
 10% find the frequency response characteristics as in figures (7.b) & (7.c)

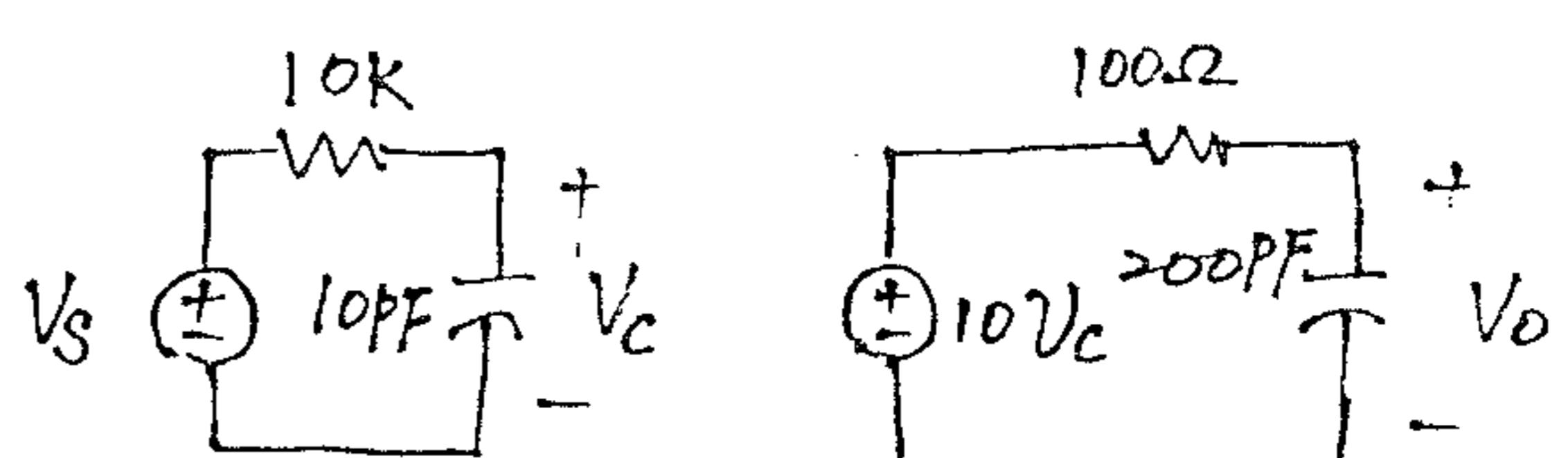


Fig (7.a)

