系別:機械與機電工程學系

科目:動態系統

准帶項目請打「V」 簡單型計算機 本試題共 2 頁 ~ 【

You may make some assumptions if necessary. Please write down your answer clearly.

- (1) What is the similarity in dynamic systems? Please give an example. (20%)
- (2) Obtain the transfer functions $X_1(s)/U(s)$ of the mechanical system shown in Figure 1. (20%)

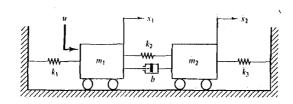


Figure 1.

(3) Obtain the transfer functions $X_0(s)/X_i(s)$ of the mechanical system shown in Figure 2. (20%)

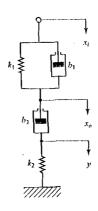


Figure 2.

淡江大學 95 學年度碩士班招生考試試題

67-2

系別:機械與機電工程學系

科目:動態系統

(4) Please derive the transfer function for e_0 as a function of e_i of the op-amp circuit (Fig. 3). (20%)

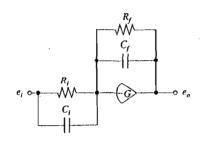


Figure 3.

(5) Obtain the dynamic equation of the open-loop DC motor speed control system (Fig. 4). (Hint: You may assume the possible constant first.) (20%)

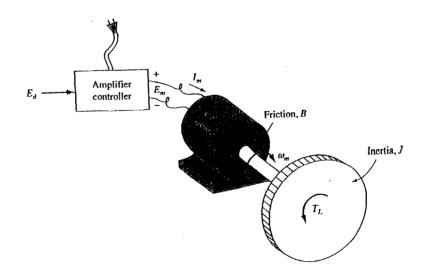


Figure 4.